

CSE350


Ahmad Zubair

Sec: 07

19101147

Report:

1.

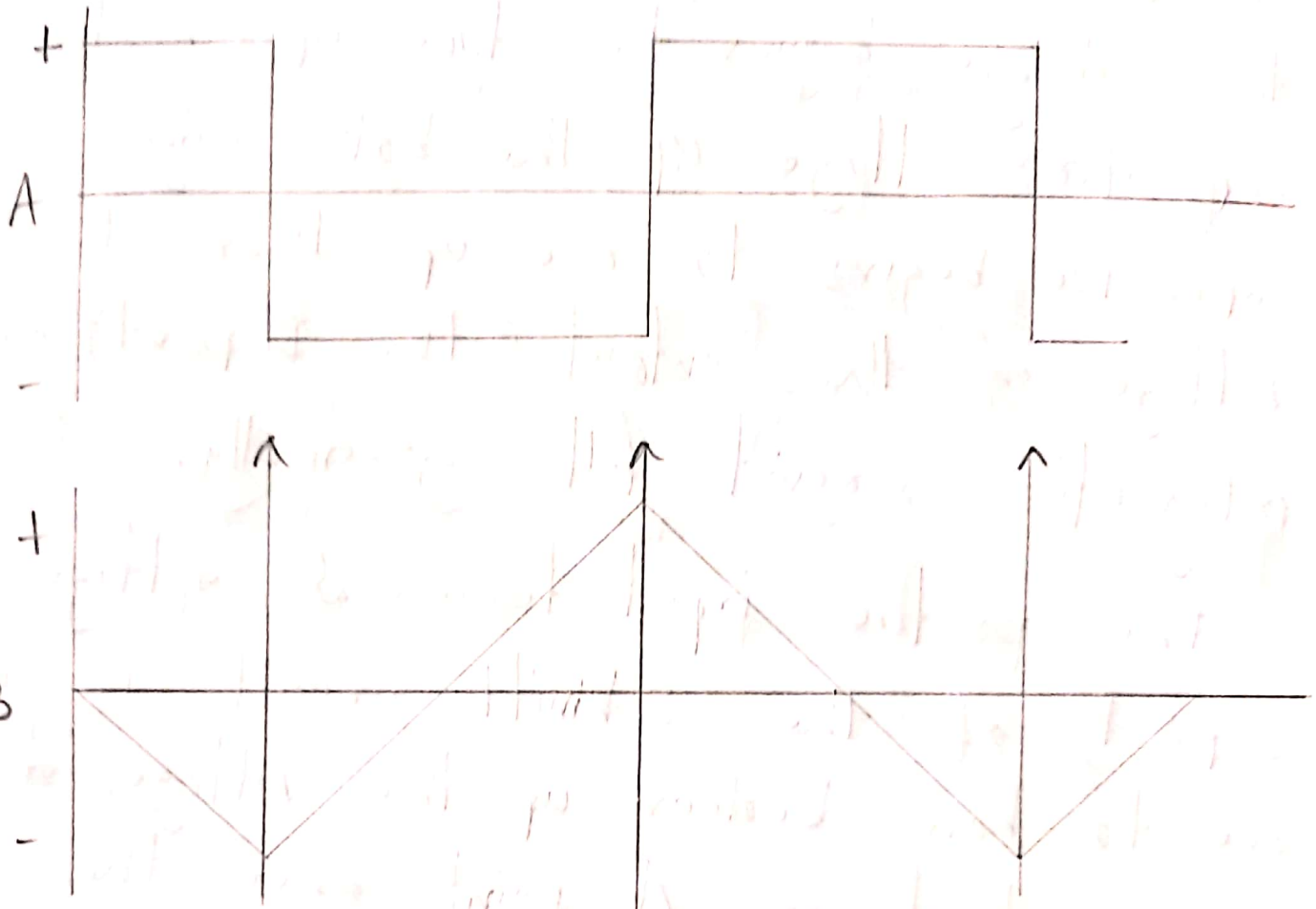

2. The circuit is composed of the Schmitt circuit and the integration circuit.

In case of turning on, the output (the A point) of the Schmitt circuit becomes the positive or negative saturated voltage.

The electric current move through the

19101147

capacitor  $C$  through the resistor  $R_1$  when the A point becomes positive. When the electric charge begins to store up in the capacitor, voltage of the both edges of the capacitor begins to rise up, then the voltage of the output (the B point) of the integration circuit falls gradually.

The positive input terminal voltage (the C point) of the Schmitt circuit is the one to have broken up the voltage difference between A point and the B point with the resistors  $R_2$  and  $R_3$ . The voltage of the C point goes down as well, when voltage of the B point starts to go down. The resistors  $R_2$  and  $R_3$  play a great role in determining the fall percentage.

19101147

As soon as the voltage of the C point falls below 0V, the voltage of the output (the A point) of the Schmitt circuit changes into the minus very fast. For the voltage of the C point to fall below 0V, the condition of  $R_2$  being greater than  $R_3$  is necessary. After that, the flow of electric current to the capacitor C reverses and the electric current moves through the direction of the point A through the resistor  $R_1$ . Because of this, the voltage of the B point rises up gradually.

When the voltage of the C point surpasses 0V, the output (the A point) of the Schmitt circuit changes into the plus rapidly. This makes the B

19101147

Point change to the direction of the negative. Here also, the condition of  $R_2$  being greater than  $R_3$  helps the voltage of the C point to surpass 0V. Lastly, the repetition of the above mentioned steps get us the square wave as the output of the A point and the triangular wave as the output of B point.

3. No, the integrator circuit can't be implemented with an inductor.



19101147

$$\text{Theoretical frequency} = \left( \frac{1}{4 \times R_1 \times C} \right) \left( \frac{R_2}{R_3} \right)$$

$$= \frac{1}{4 \times 10 \times 10^3 \times 0.4 \times 10^{-6}} \times \frac{10 \times 10^3}{4 \times 10^3}$$

$$= 156.25 \text{ Hz}$$

Experimental time period,  $T = 6.5 \text{ ms}$

$$\therefore \text{Experimental frequency, } f = \frac{1}{6.5 \times 10^{-3}}$$
$$= 153.8461 \text{ Hz}$$

Theoretical Frequency	Experimental Time Period, $T(\text{ms})$	Experimental frequency, $F(\text{Hz})$
156.25	6.5	153.8461

