

CSE350

Ahmad Zubair

Sec: 07

Input A	Input B	Input (VA)	Input (VB)	V0	V1	V2	V3	V4	V5	V6
0	0	0	0	4.61312	0.71735	0.00769	0	5	4.80314	5
0	1	0	5	4.61312	0.75531	0.04940	0	5	4.80314	5
1	0	5	0	4.61312	0.75531	0.04940	0	5	4.80314	5
1	1	5	5	0.00940	2.66148	1.95156	1.04597	1.13839	0.57464	4.99692

1. When the both the inputs are logical low ( $0.2\text{ V}$ ) the values of  $V_{be1}$  &  $V_{be2}$  are  $0.9\text{ V}$  which makes it the values of  $V_{b1}$  &  $V_{b2}$   $0.9\text{ V}$  as well. However to turn on the transistors,  $T3$  &  $T4$  the value needs to be  $1.4\text{ V}$ . As a result, both  $T3$  &  $T4$  are in cutoff mode. On the other hand, there's current flow from  $V_{cc}$  to  $V_o$  through the transistor,  $T5$  & the diode,  $D1$ . So, the output is logical high ( $3.3\text{ V}$  to  $4.0\text{ V}$ ).


We get logical high as output whenever there's at least one low input.

On the other hand, when both the inputs are logical high ( $5\text{ V}$ ), the value is enough for the transistors,  $T3$  &  $T4$  to turn on which is greater than equal to  $1.4\text{ V}$ . However, the value of  $V_{be5}$  is not enough for  $T5$  to

ID-19101147

turn on. So, T5 is in cutoff mode.

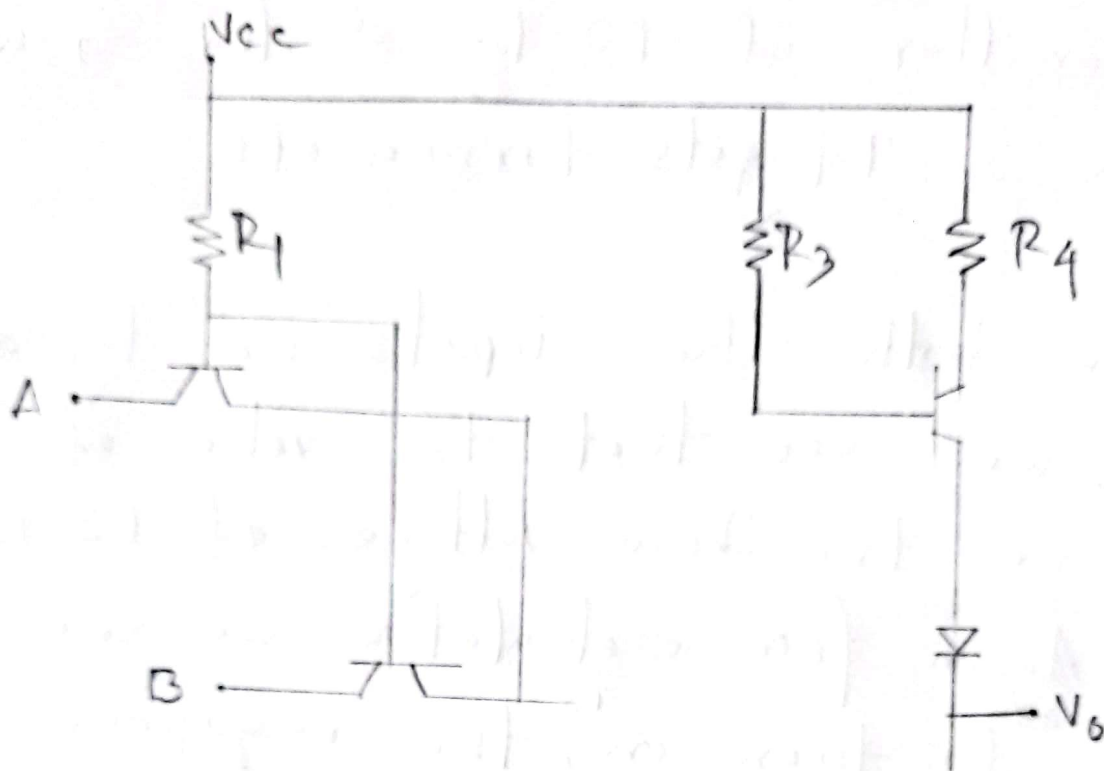2. A totem is an object serving as the emblem of a family or clan ~~to~~ and often as a reminder of its ancestry. The object is formed by sticking parts together. The output stage of this circuit is formed in such a way where the resistor comes first, then comes the transistor, after that comes the diode and finally comes another transistor. This setup seems just like a totem. That's how the name came.



4. The transistor,  $T_3$  is in phase splitter section of the TTL circuit. The job of  $T_3$  is to phase split. When the value of the base of  $T_3$  is logical low, it makes the value of the emitter of  $T_3$  logical high. As a result, when  $T_5$  is off,  $T_4$  gets turned on. On the other hand, when the value of the base of  $T_3$  is



ID-19101147

is logical high, it makes the value of the emitter of  $T_3$  logical low. So, when  $T_5$  is on,  $T_4$  gets turned off.

5. when both the inputs are logical high, we see that the value of  $V_{b3}$  i.e. the base voltage of  $T_3$  is  $0.9V$ . Again, from calculation we see that, to turn on  $T_5$  the required voltage is  $1.4V$  ( $V_{be5} = 0.7V$  and  $D1 = 0.7V$ ).

If we don't use  $D1$  then the required voltage for  $T_5$  to turn on becomes  $0.7V$ , and as  $V_{b3} = 0.9V$ , this turns  $T_5$  on. However, if that happens then the circuit doesn't act like a NAND gate anymore.



