

CSE350

Ahmad Zubair

Sec:07

OR Gate

V_A	V_B	V_{R_1}	V_{R_2}	I_{R_1}	I_{R_2}	$V_R = Y$
0	0	0	0	0	0	0
0	5	0	0.0065	0	4.41908×10^{-5}	4.41908
5	0	0.0065	0	4.41908×10^{-5}	0	4.41908
5	5	0.00327	0.00327	2.22006×10^{-5}	2.22006×10^{-5}	4.44012

AND Gate

V_A	V_B	V_{R_1}	V_{R_2}	I_{R_1}	I_{R_2}	$V_R = Y$
0	0	0.00326	0.00326	2.22006×10^{-5}	2.22006×10^{-5}	0.55988
0	5	0.00649	0	4.41908×10^{-5}	0	0.58092
5	0	0	0.00649	0	4.41908×10^{-5}	0.58092
5	5	0	0	0	0	5

Investigate the output of the circuit for the following input conditions.

V_i	V_{R1}	V_{R2}	V_{Rc}	I_1	I_2	I_B	I_c	Y
0	0.65217	4.34782	0	4.34782×10^{-5}	4.34782×10^{-5}	0	0	5
5	4.29662	5.70334	4.89188	0.0002864	5.70334×10^{-5}	0.0002294	0.0022235	0.108117

Report:

1. If we set $V_A = 0V$, $V_B = 0V$ the output is logical low.

If we set $V_A = 0V$, $V_B = 5V$ the output is also logical low.

If we set $V_A = 5V$, $V_B = 0V$ the output remains the same as case 2.

However, if we set $V_A = 5V$, $V_B = 5V$, the output is logical high.

2. If $V_A = V_B = 6V$ & $V_R = 5V$

for OR gate,

there won't be any difference as for both the diodes the value of anode will be greater than that of the cathode. So, D_1 & D_2 will work.

for AND gate,

the diodes D_1 or D_2 won't work as the value of the anode ($V_R = 5V$) will be less than the value of any of the diodes which is $6V$. As a result, D_1 & D_2 won't work.

3. The function of $R_2 = 100k$ at the base of an inverter is to control the current flow of the base terminal. To illustrate, the $100k\Omega$ resistor is connected to the base terminal so that the base terminal could channel the excessive amount of electrons from the base terminal to a lower voltage.

4. when $V_i = 0V$,

$$V_B = -0.652178V$$

$$V_E = 0V$$

$$\therefore V_{BE} = -0.652178V$$

$$\therefore V_{BE} < 0.5 \therefore \text{cutoff}$$

when $V_i = 5V$

$$I_C = 0.00222358 A$$

$$I_B = 0.000229409 A$$

We assume $P_F = 30$ is in between 40 & 120

$$\frac{I_c}{I_B} = \frac{0.00222358}{0.000229409}$$

$$= 9.6926$$

$\therefore 9.6926 < P_F \therefore$ saturation

5.

